

# Control Systems

Deep\*

## CONTENTS

### 1 Feedback Voltage Amplifier: Shunt-Shunt

#### 1 FEEDBACK VOLTAGE AMPLIFIER: SHUNT-SHUNT

The circuit in Fig. 1.1 utilizes a voltage amplifier with gain  $\mu$  in a shunt-shunt feedback topology with the feedback network composed of resistor  $R_F$ . In order to be able to use the feedback equations you should first convert the signal source to its Norton Representation.

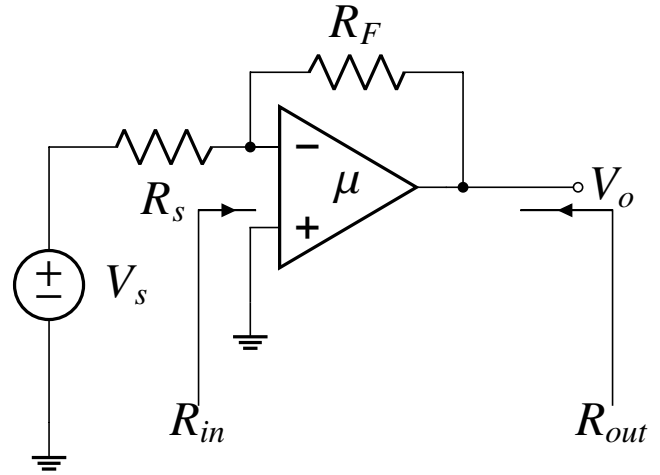


Fig. 1.1

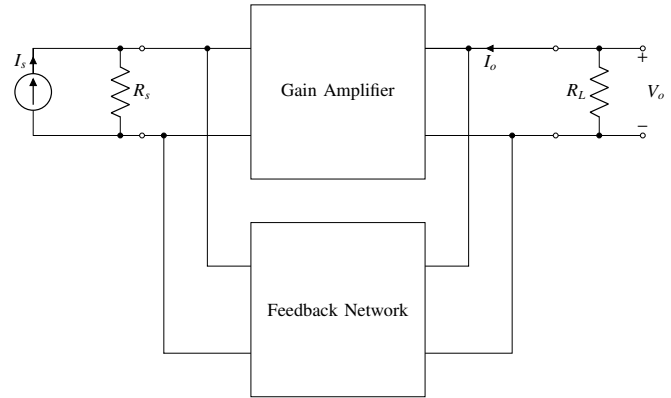


Fig. 1.2: Shunt Shunt Amplifier Block Diagram

- 1) If the loop gain is very large, what approximate closed loop voltage gain  $V_o/V_s$  is realized? If  $R_s = 1\text{k}\Omega$ , give the value of  $R_F$  that will result in  $V_o/V_s \simeq -10\text{V/V}$ .
- 2) If the amplifier  $\mu$  has a dc gain of  $10^3 \text{ V/V}$ , an input resistance  $R_{id} = 100\text{k}\Omega$ , and an output resistance  $r_o = 1\text{k}\Omega$ , find the actual  $V_o/V_s$  realized. Also find  $R_{in}$  and  $R_{out}$ .

1. Fig. 1.1 shows the original circuit. Draw the Norton Representation, A-Circuit and H-Circuit.

**Solution:** See Fig. 1.3 for the Norton Representation, Fig. 1.4 and Fig. 1.5 for A-Circuit and Fig. 1.6 for the H-Circuit.

2. Refer Table 2 for the parameters.
3. Write all the feedback equations based on all the Figs. using KCL/KVL.

**Solution:** The equations are as follows:

$$T = \frac{V_o}{I_s} = \frac{G}{1 + GH} \quad (3.1)$$

$$H = \frac{I_f}{V_o} = -\frac{1}{R_F} \quad (3.2)$$

$$I_i = I_s - I_f = \frac{I_s}{1 + GH} \quad (3.3)$$

$$R_{if} = \frac{V_i}{I_s} = \frac{V_i}{(1 + GH)I_i} = \frac{R_i}{1 + GH} \quad (3.4)$$

$$R_{of} = \frac{R_o}{1 + GH} \quad (3.5)$$

$$R_{in} = \frac{1}{\frac{1}{R_{if}} - \frac{1}{R_s}}, R_{out} = \frac{1}{\frac{1}{R_{of}} - \frac{1}{R_L}} \quad (3.6)$$

\*The author is with the Department of Electrical Engineering, Indian Institute of Technology, Hyderabad 502285 India. All content in this manual is released under GNU GPL. Free and open source.

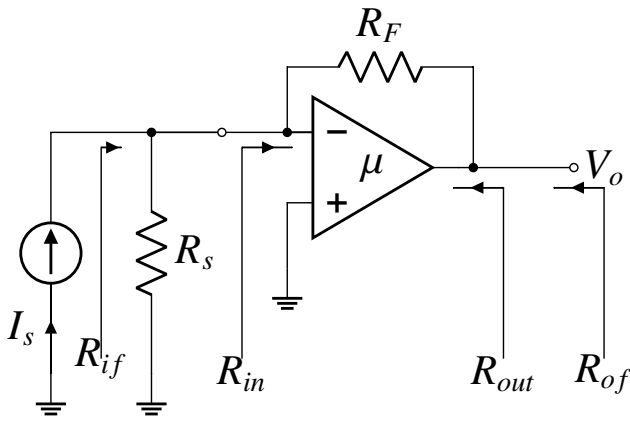


Fig. 1.3

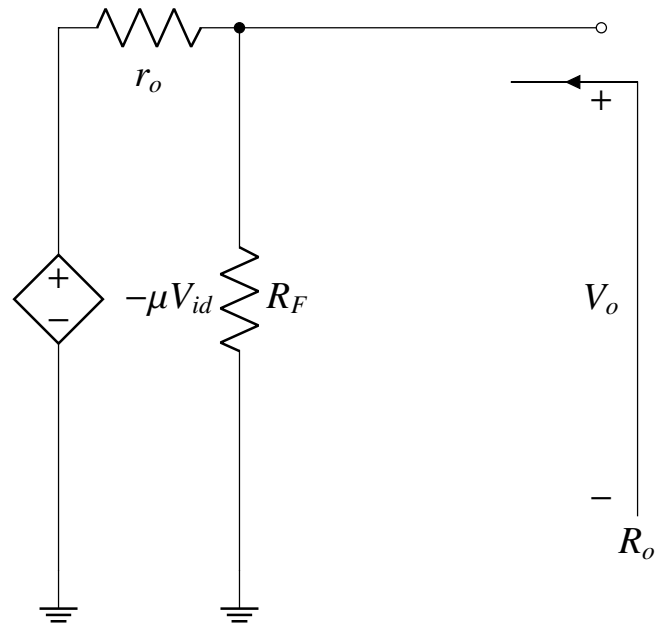


Fig. 1.5

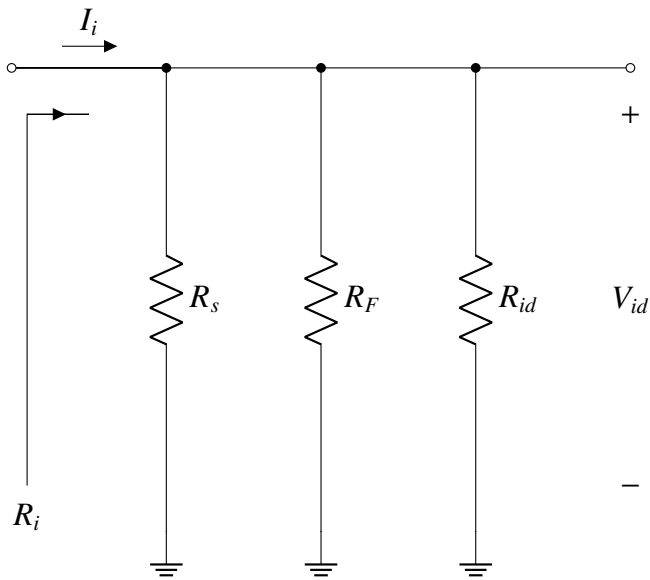


Fig. 1.4

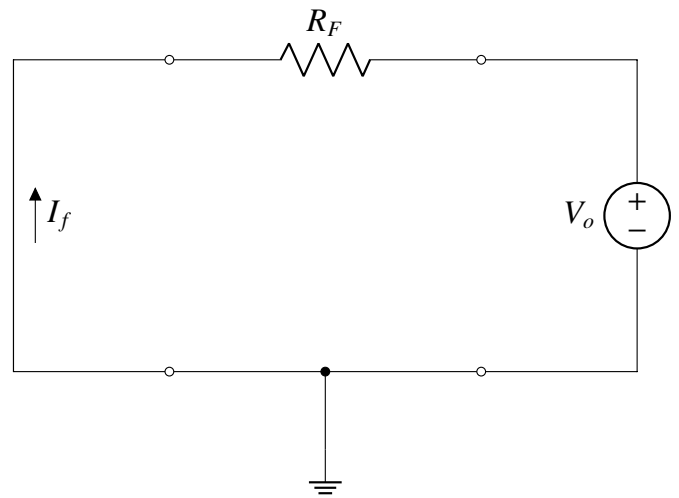


Fig. 1.6

4. If the loop gain is very large, what approximate closed-loop voltage gain  $V_o/V_s$  is realized? Also if  $R_s = 1 \text{ k}\Omega$ , give the value of  $R_F$  that will result in  $V_o/V_s \approx -10 \text{ V/V}$ .

**Solution:** If the loop gain  $GH$  is very large then the closed loop gain is,

$$T = \frac{V_o}{I_s} = \frac{G}{1 + GH} \quad (4.1)$$

$$\because GH \gg 1 \Rightarrow T \approx \frac{1}{H} \quad (4.2)$$

From equation 3.2 and 4.2 we get,

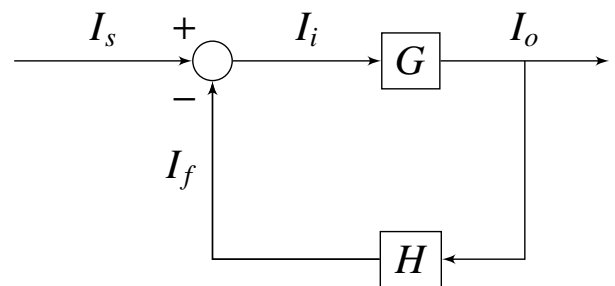


Fig. 1.7: Block Diagram

$$T \approx -R_F \quad (4.3)$$

$$\Rightarrow \frac{V_o R_s}{V_s} \approx -R_F \quad (4.4)$$

$$\Rightarrow R_F = 10 \text{ k}\Omega \quad (4.5)$$

Parameters	Description
$G$	Open Loop Gain
$H$	Feedback Factor
$T$	Closed Loop Gain
$V_0$	Output Voltage
$V_s$	Signal Source Voltage
$V_{id}$	Input Voltage of Opamp
$I_s$	Signal Source Current
$I_f$	Feedback Current
$R_i$	Total Input Resistance
$R_{out}$	Total Output Resistance
$R_{id}$	Input resistance of Opamp
$r_o$	Output resistance of Opamp
$R_i$	Input resistance of Open Loop
$R_o$	Output resistance of Open Loop
$R_{if}$	Input resistance of Feedback
$R_{of}$	Output resistance of Feedback
$R_s$	Resistance of Current Source
$V_f$	Voltage across $R_s$
$V_{in}$	Voltage at -ve terminal of opamp
$f$	Closed loop 3-dB freq.

TABLE 2

5. If the amplifier  $\mu$  has a dc gain of  $10^3$  V/V, an input resistance  $R_{id} = 100$  k $\Omega$ , and an output resistance  $r_o = 1$  k $\Omega$ , find the actual  $V_o/V_s$  realized. Also find  $R_{in}$  and  $R_{out}$ .

**Solution:** To find  $V_o/V_s$ ,  $R_{in}$  and  $R_{out}$  first find the other necessary parameters. From Fig. 1.4 we get,

$$R_i = R_{id} || R_F || R_s \quad (5.1)$$

$$R_i = 100k || 10k || 1k = 0.90k\Omega \quad (5.2)$$

$$V_{id} = I_i R_i \quad (5.3)$$

From Fig. 1.5 we get,

$$R_o = r_o || R_F \quad (5.4)$$

$$\Rightarrow R_o = 1k || 10k = 0.91k\Omega \quad (5.5)$$

$$V_o = -\mu V_{id} \frac{R_F}{r_o + R_F} \quad (5.6)$$

From equation 5.3 and 5.6 we get the open-loop gain as,

$$G = \frac{V_o}{I_i} = -\mu R_i \frac{R_F}{r_o + R_F} \quad (5.7)$$

$$\Rightarrow G = -(1000)(0.90) \frac{10}{11} = -819.00k\Omega \quad (5.8)$$

From equation 3.2 and 5.8 we get closed loop gain T as,

$$T = \frac{G}{1 + GH} = \frac{-819}{82.9} = -9.88k\Omega \quad (5.9)$$

From equation 3.1 we know,

$$T = \frac{V_o}{I_s} \quad (5.10)$$

$$\Rightarrow T = \frac{V_o R_s}{V_s} \quad (5.11)$$

$$\Rightarrow \frac{V_o}{V_s} = \frac{T}{R_s} \quad (5.12)$$

$$\Rightarrow \frac{V_o}{V_s} = \frac{-9.88}{1} = -9.88V/V \quad (5.13)$$

From equation 3.4 and 3.6 we know,

$$R_{if} = \frac{R_i}{1 + GH} = \frac{0.90}{82.9} \quad (5.14)$$

$$\Rightarrow R_{if} = 10.87\Omega \quad (5.15)$$

$$R_{in} = \frac{1}{\frac{1}{R_{if}} - \frac{1}{R_s}} \quad (5.16)$$

$$\Rightarrow R_{in} = \frac{1}{\frac{1}{10.87} - \frac{1}{1000}} = 10.99\Omega \quad (5.17)$$

Because  $R_L$  is not there in the circuit so we take its value as  $\infty$ , so from equation 3.5 and 3.6 we know,

$$R_{of} = \frac{R_o}{1 + GH} = \frac{0.91}{82.9} \quad (5.18)$$

$$\Rightarrow R_{of} = 10.97\Omega \quad (5.19)$$

$$R_{out} = \frac{1}{\frac{1}{R_{of}} - \frac{1}{R_L}} \quad (5.20)$$

$$\Rightarrow R_{out} = \frac{1}{\frac{1}{10.97} - \frac{1}{\infty}} = 10.97\Omega \quad (5.21)$$

Verify the above calculations using the following Python code.

```
codes/ee18btech11011/ee18btech11011_cal.
```

ipynb

6. If the amplifier  $\mu$  has an upper 3-dB frequency of 1 kHz and a uniform -20-dB/decade gain rolloff, what is the 3-dB frequency of the gain  $|V_o/V_s|$ .

**Solution:** To find the 3-dB frequency i.e.,  $\omega_{3dB}$  we need to look at the Fig.6.8.

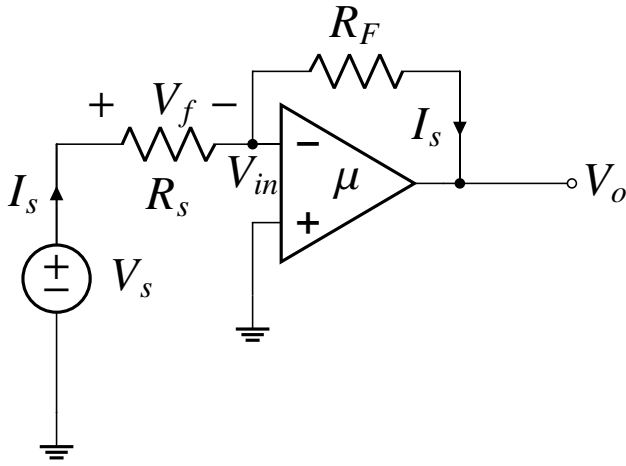


Fig. 6.8

The open loop gain  $G$  is given as follows in terms of frequency:

$$G = \frac{\mu}{1 + \frac{jf}{f_c}} \quad (6.1)$$

From Fig.6.8 we can say that:

$$V_{in} = V_s - V_f \quad (6.2)$$

$$V_o = -GV_{in} \quad (6.3)$$

$$\frac{V_f}{R_s} = \frac{V_{in} - V_o}{R_F} \quad (6.4)$$

From equation 6.3 and 6.4 we get:

$$\frac{V_f}{R_s} = \frac{-\frac{V_o}{G} - V_o}{R_F} \quad (6.5)$$

$$\Rightarrow \frac{V_f}{V_o} = -\frac{(1 + G)(R_s)}{G(R_F)} = -H \quad (6.6)$$

$$\because G \gg 1 \Rightarrow H = \frac{R_s}{R_F} \quad (6.7)$$

Now from equation 6.2, 6.3 and 6.6 we get:

$$-\frac{V_o}{G} = V_s + HV_o \quad (6.8)$$

$$\Rightarrow \frac{V_o}{V_s} = -\frac{G}{1 + GH} \quad (6.9)$$

Now, for "f" to be 3-dB frequency given condition should match i.e.,:

$$\left| \frac{V_o}{V_s} \right| = \frac{1}{\sqrt{2}} \quad (6.10)$$

$$\Rightarrow \left| -\frac{G}{1 + GH} \right| = \frac{1}{\sqrt{2}} \quad (6.11)$$

$$\Rightarrow \frac{\frac{\mu}{1 + \frac{jf}{f_c}}}{1 + \frac{(R_s)}{(R_F)} \frac{\mu}{1 + \frac{jf}{f_c}}} = \frac{1}{\sqrt{2}} \quad (6.12)$$

Parameters	Values
$R_s$	1k $\Omega$
$R_F$	10k $\Omega$
$\mu$	1000
$f_c$	1kHz

TABLE 6

Now putting the appropriate values as given in Table 6 we get:

$$\frac{\frac{1000}{1 + \frac{jf}{1000}}}{1 + \frac{(1)}{(10)} \frac{1000}{1 + \frac{jf}{1000}}} = \frac{1}{\sqrt{2}} \quad (6.13)$$

$$\frac{f^2}{10^{12}} + \frac{101^2}{10^6} = 2 \quad (6.14)$$

$$\Rightarrow f \approx 1.41 \text{ MHz} \quad (6.15)$$

7. Using ngspice verify the Closed-Loop Transfer function or  $V_o/V_s$ .

**Solution:** From 5.13 we know that:

$$\frac{V_o}{V_s} = -9.88 \text{ V/V} \quad (7.1)$$

So, to verify this use the following spice file.

spice/ee18btech11011/ee18btech11011.net

and finally to get the result use the following python code.

spice/ee18btech11011/ee18btech11011\_spice.py

Result:

```
figs/ee18btech11011/  
ee18btech11011_spice_result.eps
```

Following are the instructions to run the spice file.

```
spice/ee18btech11011/README.md
```